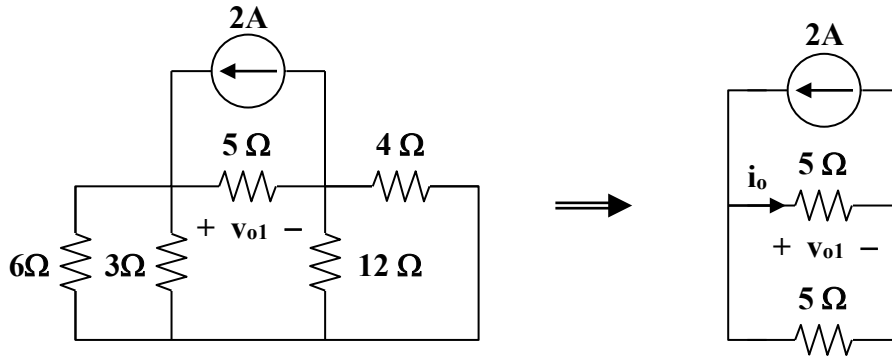


### Solution 4.12


Let  $v_o = v_{o1} + v_{o2} + v_{o3}$ , where  $v_{o1}$ ,  $v_{o2}$ , and  $v_{o3}$  are due to the 2-A, 12-V, and 19-V sources respectively. For  $v_{o1}$ , consider the circuit below.



$6||3 = 2$  ohms,  $4||12 = 3$  ohms. Hence,

$$i_o = 2/2 = 1, v_{o1} = 5i_o = 5 \text{ V}$$

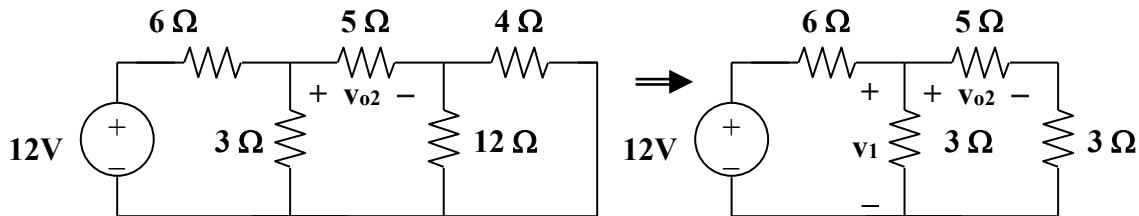
For  $v_{o2}$ , consider the circuit below.



$$3||8 = 24/11, v_1 = [(24/11)/(6 + 24/11)]12 = 16/5$$

$$v_{o2} = (5/8)v_1 = (5/8)(16/5) = 2 \text{ V}$$

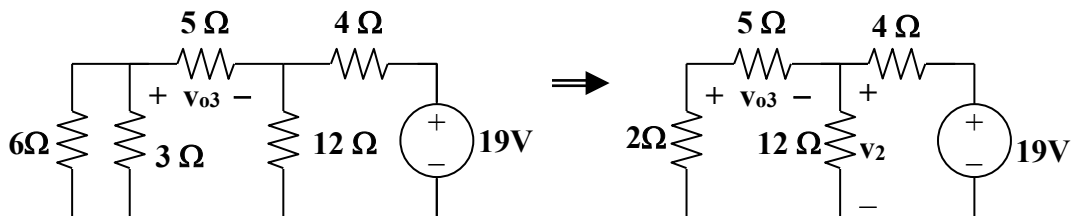For  $v_{o3}$ , consider the circuit shown below.



$$7||12 = (84/19) \text{ ohms}, v_2 = [(84/19)/(4 + 84/19)]19 = 9.975$$

$$v = (-5/7)v_2 = -7.125$$

$$v_o = 5 + 2 - 7.125 = -125 \text{ mV}$$

### Solution 4.27


Transforming the voltage sources to current sources gives the circuit in Fig. (a).

$$10\parallel 40 = 8 \text{ ohms}$$


Transforming the current sources to voltage sources yields the circuit in Fig. (b).  
Applying KVL to the loop,

$$-40 + (8 + 12 + 20)i + 200 = 0 \text{ leads to } i = -4$$

$$v_x = 12i = \mathbf{-48 \text{ V}}$$

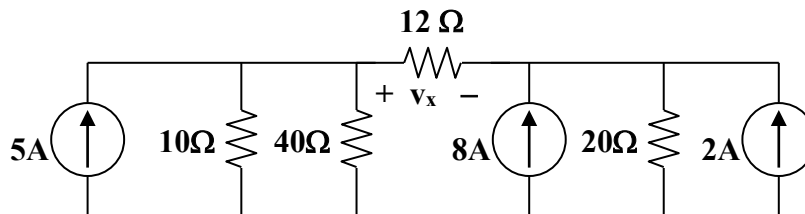


(a)

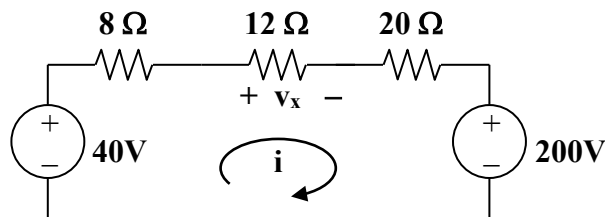

(b)

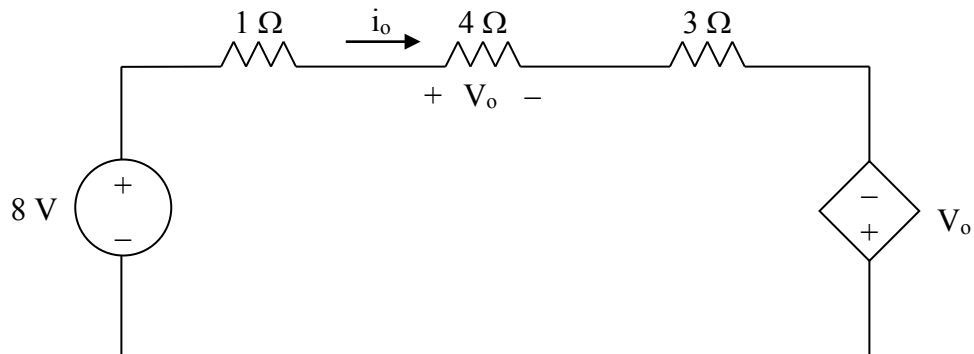**Solution 4.28**

Convert the dependent current source to a dependent voltage source as shown below.



Applying KVL,

$$-8 + i_o(1 + 4 + 3) - V_o = 0$$

But  $V_o = 4i_o$

$$-8 + 8i_o - 4i_o = 0 \quad \longrightarrow \quad i_o = \underline{2\text{ A}}$$

### Solution 4.39

Obtain the Thevenin equivalent at terminals a-b of the circuit shown in Fig. 4.106.


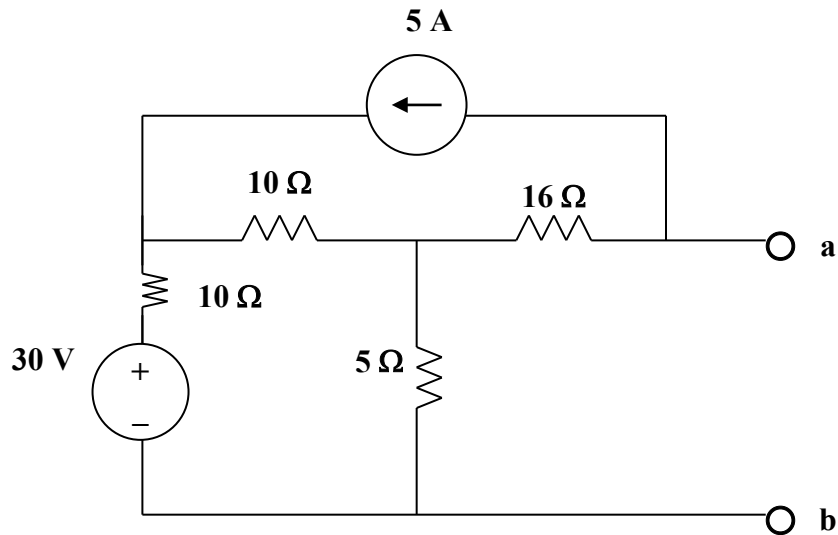


Figure 4.106  
For Prob. 4.39.
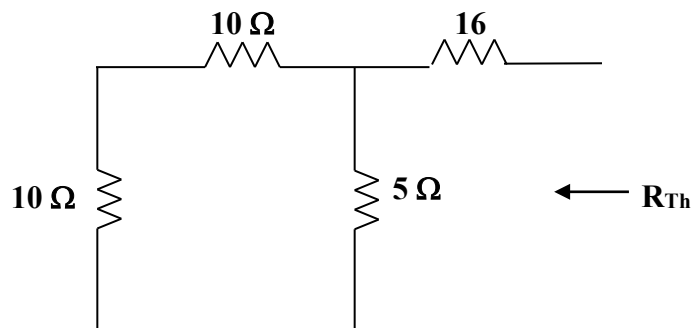
### Solution

We obtain  $R_{Th}$  using the circuit below.



$$R_{Th} = 16 + (20 \parallel 5) = 16 + (20 \times 5) / (20 + 5) = 20 \, \Omega$$

To find  $V_{Th}$ , we use the circuit below.

### Solution 4.48

Determine the Norton equivalent at terminals **a-b** for the circuit in Fig. 4.115.


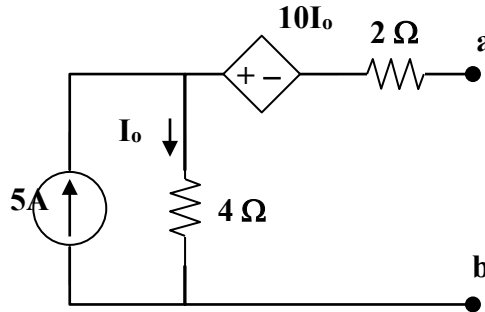


Figure 4.115  
For Prob. 4.48.
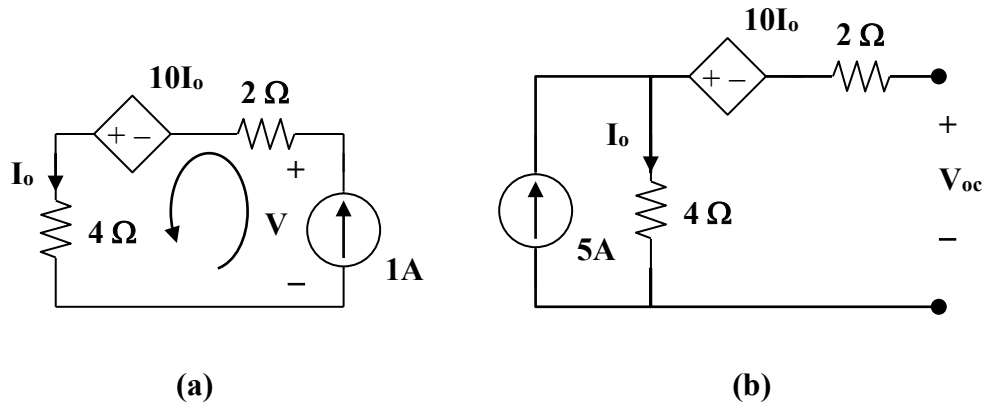
### Solution

To get  $R_{Th}$ , consider the circuit in Fig. (a).



From Fig. (a),  $I_o = 1$ ,  $6 - 10 - V = 0$ , or  $V = -4$


$$R_{eq} = V/1 = -4 \text{ ohms}$$

Note that the negative value of  $R_{eq}$  indicates that we have an active device in the circuit since we cannot have a negative resistance in a purely passive circuit.

To solve for  $I_N$  we first solve for  $V_{oc}$ , consider the circuit in Fig. (b),

$$I_o = 5, V_{oc} = -10I_o + 4I_o = -30 \text{ V}$$

$$I_N = V_{oc}/R_{eq} = 7.5 \text{ A.}$$

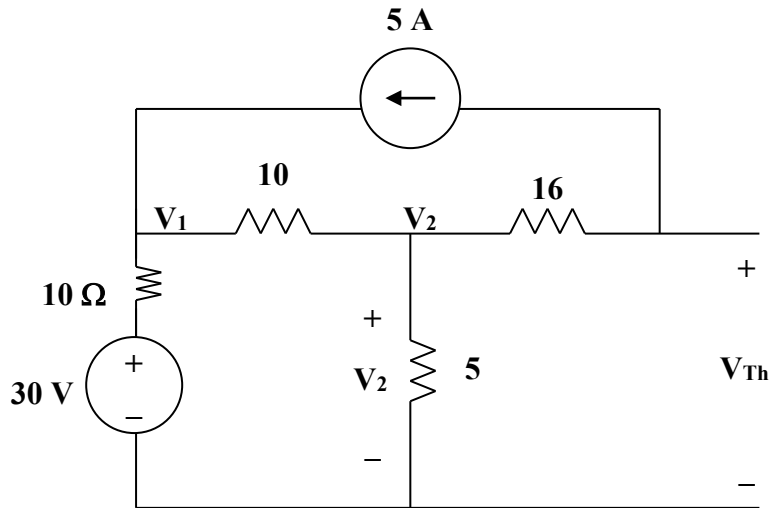


At node 1,  $[(V_1 - 30)/10] + [(V_1 - V_2)/10] - 5 = 0$  or  $[0.1 + 0.1]V_1 - 0.1V_2 = 8$  (1)

At node 2,  $[(V_2 - V_1)/10] + [(V_2 - 0)/5] + 5 = 0$  or  $-0.1V_1 + 0.3V_2 = -5$  (2)

Adding 3x(1) to (2) gives  $(0.6 - 0.1)V_1 = 19$  or  $V_1 = 19/0.5 = 38$  and  $V_2 = (-5 + 0.1 \times 38)/0.3 = -4$  V.

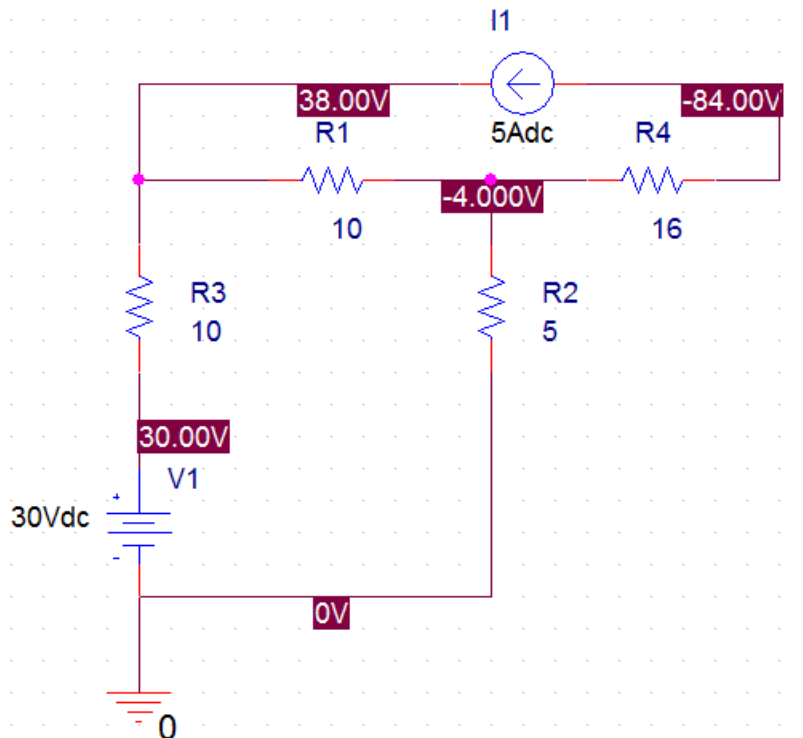Finally,  $V_{Th} = V_2 + (-5)16 = -4 - 80 = -84$  V. Checking with PSpice we get,



### Solution 4.72

- For the circuit in Fig. 4.138, obtain the Thevenin equivalent at terminals **a-b**.
- Calculate the current in  $R_L = 13\ \Omega$ .
- Find  $R_L$  for maximum power deliverable to  $R_L$ .
- Determine that maximum power.

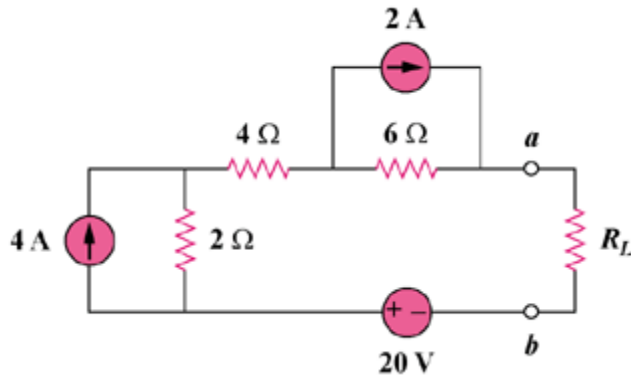



Figure 4.138  
For Prob. 4.72.

### Solution

- $R_{Th}$  and  $V_{Th}$  are calculated using the circuits shown in Fig. (a) and (b) respectively.

From Fig. (a),  $R_{Th} = 2 + 4 + 6 = 12\ \text{ohms}$

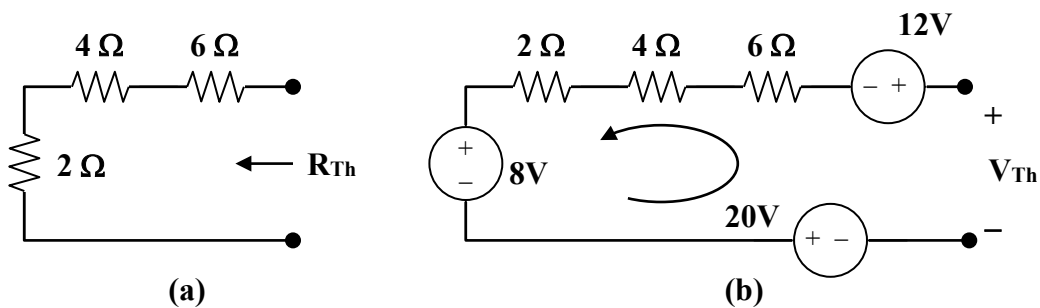From Fig. (b),  $-V_{Th} + 12 + 8 + 20 = 0$ , or  $V_{Th} = 40\ \text{V}$



- $i = V_{Th}/(R_{Th} + R) = 40/(12 + 13) = 1.6\ \text{A}$
- For maximum power transfer,  $R_L = R_{Th} = 12\ \text{ohms}$
- $p = V_{Th}^2/(4R_{Th}) = (40)^2/(4 \times 12) = 33.33\ \text{watts}.$